

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total number of pages:[1]

**B.Tech. || ECE || 6<sup>th</sup> Sem**  
**Digital System Design**  
**Subject Code: BTEC-904**  
**Paper ID:**

**Time allowed: 3 Hrs**

**Max Marks: 60**

**Important Instructions:**

- All questions are compulsory

**PART A (10x 2marks)**

Q. 1. Short-Answer Questions:

- What do you mean by Hazards?
- What is a multiplier?
- Compare synchronous counters with asynchronous counters.
- What is the difference between MUX and DEMUX?
- How will you classify adders?
- Differentiate PAL & PLA.
- What is FPGA?
- Define FSM.
- What is difference between latch and Flip-flop?
- List various types of ROM.

**PART B (5x8marks)**

Q. 2. Write note on Moore and Mealy machines.

CO3

OR

What do you mean by FSM? Explain its limitations.

CO3

Q. 3. Write notes on FPGA.

CO4

OR

Design a BCD to Excess-3 code converter using PLA.

CO4

Q. 4. Implement Full adder using MUX.

CO1

OR

Can we use Adder as Subtractor? If yes, explain how?

CO1

Q. 5. Design a counter that count in sequence 0-1-2-3-4 and back to initial state using D flip-flops. The counter must avoid lock-out condition.

CO2

OR

What is Flip-flop? Design a clocked SR Flip-flop.

CO2

Q. 6. Explain in detail the working of JK flip-flop. Convert SR flip-flop to JK flip-flop.

CO2

OR

Explain ASM charts by taking suitable example.

CO2