

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total number of pages: [1]

Total number of questions: 06

B.Tech. || ECE || 3rd Sem

Analog Devices & Circuits

Subject Code: BTEC-302A/301

(RP)

Paper ID: M/18

(2011 batch onwards)

Time allowed: 3 Hrs

Important Instructions:

Max Marks: 60

- All questions are compulsory.
- Assume any missing data

PART A (2×10)

Q. 1. Short-Answer Questions:

- (a) How the depletion layer is formed?
- (b) Explain the V-I characteristics of Zener Diode.
- (c) Compare CB, CE and CC parameters.
- (d) Write a short note on Schottky diode.
- (e) What is Barkhausen's Criteria?
- (f) Compare UJT and BJT and give one example of each.
- (g) Draw the dissipation curve.
- (h) Compare Positive and negative Feedback.
- (i) Design a cheapest Oscillator with minimum number of components.
- (j) Explain Tunneling effect with two applications.

PART B (8×5)

- Q. 2. Explain in detail working principal and characteristics of Tunnel Diode. CO1
OR
Design a power supply using Zener diode as a voltage regulator. CO1
- Q. 3. Explain the design of CE amplifier with voltage divider biasing circuit. CO2
OR
Draw the circuit diagram of Emitter follower and discuss its applications. CO2
- Q. 4. Explain in detail the working of Complimentary Push Pull amplifier. CO3
OR
Explain in detail the Voltage series Feedback amplifier. CO3
- Q. 5. Explain the construction, working, efficiency and distortion analysis of Transformer coupled audio amplifier. CO3
OR
Explain the design of Wein bridge Oscillator and its applications? CO3
- Q. 6. Design h model of Transistor amplifier in CE mode. CO4
OR
Explain and prove Miller's Theorem. CO4