

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

 Total number of pages: [02]  
 Total number of questions: 06

**B.Tech. || ECE || 3<sup>rd</sup> Semester**  
**Network Analysis and Synthesis**  
**Subject Code: BTEC-303**

Time allowed: 3 Hrs

Max Marks: 60

**Important Instructions:**

- All questions are compulsory
- Assume any missing data

**PART A (2×10)**

All COs

Q. 1. Short-Answer Questions:

- Explain the term network analysis.
- Differentiate between loop and node.
- State and explain Reciprocity Theorem
- Define unit step function and find its Laplace transform.
- How will you define transfer function? Explain.
- List the demerits of m-derived filters.
- Define Kirchhoff's current Law.
- Define a positive real function.
- What is Gate function?
- Differentiate between loop analysis and nodal analysis.

**PART B (8×5)**

Q. 2. State and prove the Thevenin's theorem with the help of a suitable example and also write limitations. COa

OR

Q. 3. What is standard signals? Explain all the functions of standard signals with example. COa  
 What is transfer function? Explain time domain behaviors from poles and zeros. COb

OR

Q. 4. State and Prove the convolution theorem with example. COb  
 Find the Foster-I and Foster-II form of the function COc

$$Z(s) = (s + 1)(s + 3) / s(s + 2)$$

OR

Q. 5. What are the properties of R-C driving point impedance functions? How these can be synthesized? COc

Q. 5. Define composite filter. Draw the block diagram of composite filter and explain each stage in detail. COd

OR

What is a filter? Give the properties of filter. Classify the filters depending upon the  $\alpha$  and  $\beta$  relationship between the arm impedances. Derive the expressions for characteristic impedance of a low pass filter in the pass band and stop band. COd

Q. 6. How is two terminal pair network characterized in terms of input output variables? Also mention various two port parameters and write equations in terms of these parameters.

OR

Design a constant  $-K$  band stop filter with cut-off frequencies of 3kHz and 7.5kHz and nominal characteristic impedance of  $R_o = 900\Omega$ . COc