

52+0=52  
47+2=49

SHAHEED BHAGAT SINGH STATE TECHNICAL CAMPUS, FEROZEPUR

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total number of pages: |1|

B.Tech. || EE || 4<sup>th</sup> Sem

Digital Electronics

(RG/RP)

Subject Code: BTEE-405A/BTEC-404

Paper ID: M/18

(2011 batch onwards)

Time allowed: 3 Hrs

Max Marks: 60

Important Instructions:

- All questions are compulsory

PART A (10x 2marks)

Q. 1. Short-Answer Questions:

- Compare TTL with ECL.
- What is the difference between MUX and DEMUX?
- Compare synchronous counters with asynchronous counters.
- Differentiate encoder and decoder.
- Differentiate half and full adder.
- What is Ring Counter?
- Convert binary to octal code (110011).
- What is Shift Register?
- What do you mean by Resolution of ADC?
- What are different minimization techniques?

PART B (5x8marks)

Q. 2. Solve the following function using K-map.

$$F(A, B, C, D) = \sum m(0, 1, 2, 5, 6, 8, 10, 12, 13, 14)$$

OR

What are Universal Gates? Prove that NAND and NOR are Universal gates.

Q. 3. Can we use Adder as Subtractor? If yes, explain how?

OR

Implement Full adder using 8:1 MUX.

Q. 4. What is Flip-flop? Design a clocked T Flip-flop.

OR

Explain in detail the working of JK flip-flop. Convert T flip-flop to D flip-flop.

Q. 5. Explain the working of Parallel Comparator type A/D converter.

OR

With help of neat diagram explain working of R-2R ladder type DAC.

Q. 6. Implement BCD to Seven segment Display Driver/Decoder.

OR

Design a BCD to Excess-3 code converter.

CO1

CO1

CO2

CO2

CO3

CO3

CO4

CO4

CO2

CO2