

**B.Tech. || ECE || 3<sup>rd</sup> Sem**  
**Analog Devices & Circuits**  
**Subject Code: BTEC-302A**  
**Paper ID: (for office use)**

**Time allowed: 3 Hrs**  
**Important Instructions:**

- All questions are compulsory
- Assume any missing data

**Max Marks: 60**

**PART A (2×10)**

**Q.1**

- i. What do you mean by reverse recovery time of diode?
- ii. Explain the role of heat sink in a transistor.
- iii. What is thermal runaway of BJT?
- iv. What do you mean by peak inverse voltage of a diode?
- v. Which diode can be used as variable capacitor and how?
- vi. Draw the circuit diagram of fixed biasing.
- vii. What is stability factor?
- viii. How does the trans-conductance vary with drain current of a MOSFET?
- ix. What is Barkhausen's Criteria?
- x. Give the difference between low frequency model and high frequency model of a transistor.

**PART B (8×5)**

- Q.2**
- a. Can two back to diodes be used as transistor? Justify the answer. 4
  - b. Give the difference between avalanche and Zener breakdown. 4

**OR**

- a. Draw and explain the energy band diagrams for a PN junction diode when diode at equilibrium, forward biased and reversed biased condition. 4
  - b. Explain with neat diagram, the working of Metal oxide field effect transistor (MOSFET). Also derive the equation for the drain current of NMOS transistor. 4
- Q.3**
- a. Draw and explain the circuit diagram of potential divider biasing technique using BJT. Also derive the equation for its stability factor. 4
  - b. Given the information provided in Figure 1, determine the following: 4
- i.  $\beta$
  - ii.  $V_{CC}$
  - iii.  $R_B$

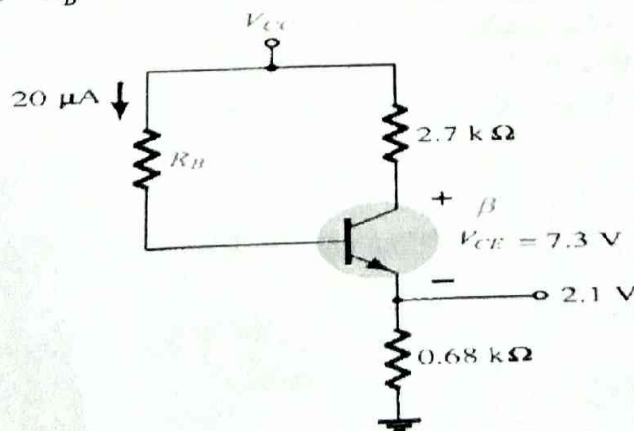


Figure 1  
Page 1 of 2

- OR**
- a. Assume that a silicon transistor with  $\beta_0=50$ ,  $V_{be}=0.6V$  and  $V_{cc}=20V$  and  $R_c=4.7k\Omega$  is used in a self-biased circuit. It is desired to establish a Q point at  $V_{ce}=8V$  and  $I_c=2mA$  and stability factor  $S$  is less than equal to 5.0. Design the circuit with all component values. 3
- b. Draw and explain the working of field effect transistor (FET). Also explain its characteristics. 4
- Q.4. a. Draw and explain the push-pull power amplifier. 4  
b. Draw and explain the working of transformer coupled audio amplifier. Also draw its frequency response. 4

- OR**
- a. Draw and explain the complimentary push-pull power amplifier. 4  
b. For the circuit of Figure 2, calculate the input power, output power, and power handled by each output transistor and the circuit efficiency for an input of 12 V rms. 4

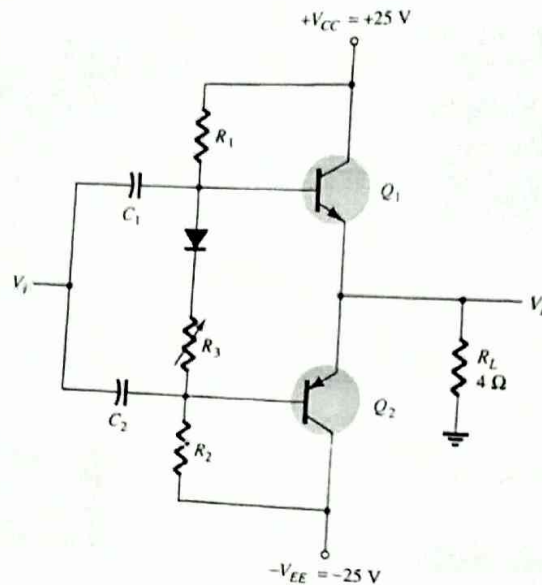


Figure 2

- Q.5 a. Draw the circuit arrangement for current series feedback. Also derive the equation for gain of the circuit. 4  
b. Draw and explain the working principle of Wein Bridge oscillator. Derive the equation for output frequency. 4
- OR**
- a. Draw and explain the working principle of RC phase oscillator. Derive the equation for output frequency. 4  
b. Colpitt oscillator is designed with  $C_1=100pF$  and  $C_2=7500pF$ . The inductance is variable. Determine the range of the inductor if the frequency of oscillation is to vary between 900kHz and 2000kHz. 4
- Q.6 Derive the transistor amplifier circuit performance in h-parameters using CE configuration. 8
- OR**
- a. The overall gain of emitter follower circuit is unity. Justify your answer with analytical equations. 4  
b. Draw and explain the four basic feedback configurations. 4