

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total number of questions: 06

Total number of pages:[2]

B.Tech. || EE || 3rd Sem

Electrical Measurements & Instrumentation

Subject Code: BTEE-303

Paper ID:

Time allowed: 3 Hrs

Max Marks: 60

Important Instructions:

- All questions are compulsory
- Assume any missing data

PART A (2×10)

All Cos

Q. 1. Short-Answer Questions:

- What are the different standards to represent EMF?
- Give limitations of PMMC instruments.
- What do you understand by air damping and eddy current damping?
- What are the advantages of instrument transformer over ammeter shunts and voltmeter multipliers?
- Mention salient features of self balancing potentiometers.
- What is meant by systematic errors?
- Comparison between Analog and Digital instruments.
- Derive the null condition of a d.c. bridge.
- What is the principle of working of flux meter?
- Give salient features of instrument transformers.
- Define burden in instrument transformers.

PART B (8×5)

Q. 2. Describe working of Hay's bridge:-Why is this bridge suited for measurement of inductance of high Q coils?

CO4

OR

Explain the Lloyd Fisher square for measurement of iron loss in a specimen of laminations.

CO4

Q. 3. Derive the equations for balance in the case of Maxwell's inductance - capacitance bridge. Draw the phasor-diagram for balance condition.

CO3

OR

- What are the essential characteristics of energy meter? Explain the working principle and give the advantages of Induction type watt hour meter. CO3
- Q. 4. Explain the circuit of a multimeter for measurement of AC voltages. CO2
OR
Discuss the procedure of standardization of a DC potentiometer CO2
- Q. 5. What are the sources of error in instrument transformers? Draw the equivalent circuit and phasor diagram of a potential transformer. CO2
OR
Discuss the working and constructional detail of dynamometer type instruments. CO2
- Q. 6. Write a short note on following: CO1
a) Wheat stone bridge
b) Self balancing potentiometer
OR
Write a short note on following: CO1
a) Current transformer.
b) Polar type AC potentiometer