

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total number of pages:[2]

B.Tech. || ECE || 3rd Sem
Analog Devices & Circuits
Subject Code: BTEC-301
Paper ID:

Time allowed: 3 Hrs

Max Marks: 60

Important Instructions:

- All questions are compulsory

PART A (10x 2marks)

- Q. 1. Short-Answer Questions:
- (a) What is Stabilization?
 - (b) Describe class A Power Amplifier.
 - (c) What is Barkhausen Criterion?
 - (d) Describe hybrid equivalent circuit.
 - (e) What is the origin of transistor?
 - (f) Differentiate between ac & dc load line.
 - (g) What do you mean by operating point?
 - (h) Describe stability factor.
 - (i) Develop relationship between α and β
 - (j) Distinguish between FET & BJT.

PART B (5×8marks)

- Q. 2. Explain the operation of Photodiode. Draw the Characteristics of the CO1 photodiode.

OR

Draw the VI Characteristics of Zener Diode and explain Zener Diode as a CO1 voltage regulator.

- Q. 3. Explain the input and output characteristics curves of a CE configuration for a CO2 transistor.

OR

Explain fixed bias circuit. In a fixed bias circuit, $R_B=150k\Omega$, $R_C=2k\Omega$, CO2 $V_{CC}=12V$. Transistor is silicon with $\beta=100$, find I_B .

- Q. 4. Discuss transistor phase inverter circuit for push pull amplifier. CO3

OR

Draw and explain the working of push pull class B amplifier. What are its CO3 advantages and disadvantages?

- Q. 5. Discuss the concept of negative feedback in amplifier in detail. CO4

OR

- Q. 6. Explain the working of a Colpitt's oscillator with a neat diagram. CO4
Explain the difference between the enhancement mode MOSFET and CO2
depletion mode MOSFETs.

OR

- Explain the working of emitter bias circuit. CO2