

Q. 5. Describe the basic circuit and principle of operation of dual converter? COc