

Roll No:.....

Total no. of Questions: 06

Time: 03 hours

Total no. of pages: 01

M.M:60

B.Tech CSE 3<sup>rd</sup> Sem  
Digital Circuits & Logic Design  
Subject Code: BTCS-303A (Paper ID: )

Note: All questions are compulsory.

**Section A (10x2marks =20)**

1. Write answers to the point
  - a) Find the dual of  $(x + y)' = x'y'$
  - b) Explain the race around condition in JK Flip Flop. How it can be eliminated.
  - c) Find the complement of  $(AB + A'B')$
  - d) Define the terms Fan-out and Noise Margin in relation to logic families.
  - e) Differentiate between Mealy and Moore machines.
  - f) Explain the CMOS inverter function.
  - g) Differentiate between synchronous and asynchronous counters.
  - h) Minimize using Boolean Algebra  $A'C' + ABC + AC' + AB'$  to two literals.
  - i) How the ROM is designated.
  - j) Draw 4-bit Serial in Serial out Shift Right Register.

**Section B – (5 x 8marks = 40)**

2.	Perform the subtraction $X-Y$ and $Y-X$ for $X = 1101$ and $Y = 1001$ using i) 1's complement ii) 2's complement OR a) Find the BCD and Excess -3 code of $(214)_{10}$ b) Convert $(333)_{10}$ into binary, octal and hexadecimal number	CO1
3.	Simply the following Boolean Function to product of sum form and implement the simplified function using NAND gates only $F(A,B,C,D) = \pi(1,3,6,9,11,12,14)$ OR Simply the following Boolean Function using QM method $F(A,B,C,D) = \sum (0,1,2,8,10,11,14,15)$	CO2
4.	Implement Full subtractor using two 4x1 muxes. OR Design 4 bit binary to gray code converter.	CO3
5.	Design synchronous BCD up counter. OR Design J-K Flip Flop using S-R Flip Flop.	CO4
6.	Explain R-2R ladder D/A converter. OR Explain counter type A/D converter.	CO5