

[illegible]

**Total number of questions: 06**

**Time allowed: 3 Hrs**

**Max Marks: 60**

- All questions are compulsory
- Assume any missing data

## All COs

- Convert Decimal Number 25 to Binary Number.
- Perform the following:  $(1010)_2 + (1111)_2$ .
- Draw the circuit of NAND and NOR gates.
- Give Associative Law.
- Which gates are called Universal gates and why?
- What are flip flops?
- Write 1's and 2's complement of  $(10101110)_2$ .
- What are combinational circuits?
- Give truth table of T flip flop.
- What will be the Binary representation of the number  $(1999)_{10}$ ?

## COI

a)  $(3A.2F)_{16} = ( )_{10}$   
 b)  $(125)_8 = ( )_{10}$   
 c)  $(34)_{16} = ( )_2$   
 d)  $(12.25)_{10} = ( )_2$

OR

What are Logic gates? Explain its types with diagram.

Q. 3. Explain Universal Properties of NAND and NOR Gates.

OR

Find the minimum sum of products expression for the function:

$$f(a,b,c,d) = \sum m(1,3,4,6,7,9,11,12,13,15)$$

Q. 4. Explain working of Master Slave JK Flip Flop.

OR

Define Multiplexer. Explain 4x1 multiplexer in detail.

Q. 5. What is RAM chip? Explain its types and working.

OR

Differentiate between PROM and EPROM.

Q. 6. Explain Half Adder and Full Subtractor with example.

OR

Apply De-Morgan's Theorem to the following expressions:

CO2

45

a)  $\overline{A + \overline{BC}}$

b)  $\overline{\overline{A} + \overline{BC} + \overline{AB}}$