

ROLL No:

--	--	--	--	--	--	--	--	--	--	--

Total number of pages:[2]

B.Tech. || ECE || 3rd Sem
Digital Electronics
Subject Code: BTEC-303A

(RP)

Paper ID: M118

(2015 batch onwards)

Time allowed: 3 Hrs

Max Marks: 60

Important Instructions:

- All questions are compulsory

PART A (10x 2marks)

Q. 1. Short-Answer Questions:

- Differentiate Combinational and sequential circuits.
- Can adder be used as a Subtractor, If yes explain how?
- Differentiate synchronous and asynchronous counters?
- What do you mean by Resolution of Digital to Analog Converter?
- Differentiate half and full adder.
- How role of MUX is different from DEMUX?
- Why NAND and NOR gates are called universal gates?
- Convert binary to Gray code (1111110011).
- List the various types of A/D converters.
- Construct the truth table for $Z = x'y + xy'$.

PART B (5x8marks)

- Q. 2. Explain the working of Counter Type A/D converter. CO4
 OR
 Explain the term Resolution, Accuracy of D/A converter. Also explain Successive approximation A/D converter. CO4
- Q. 3. Explain the working of JK flip flop, also convert RS flip flop to JK flip flop. CO3
 OR
 Explain the working of Master-Slave JK Flip-flop. CO3
 CO2
- Q. 4. Solve following function using Q-M method.
 $F(A, B, C, D) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
 OR
 How would you simplify the Boolean function $f(A, B, C, D) = C' + A'D' + BD'$ using tabulation method? CO2
- Q. 5. Design a counter that count in sequence 0-1-2-3-4 and back to initial state using D flip-flops. The counter must avoid lock-out condition. CO3
 OR
 What is Flip-flop? Design a clocked SR Flip-flop. CO3
- Q. 6. What are Signed Numbers? Subtract $(+47) - (-23)$ using two's complement CO1

subtraction method.

OR

What is Grey Code? Represent $(-57)_{10}$ in Sign magnitude, 1's complement and CO1
2's complement representation.