

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total number of pages:[1]

**B.Tech. || ECE || 4<sup>th</sup> Sem**  
**Digital System Design**  
**Subject Code: BTEC-402A**  
**Paper ID:**

Time allowed: 3 Hrs

Max Marks: 60

**Important Instructions:**

- All questions are compulsory

**PART A (10x 2marks)**

- Q. 1. Short-Answer Questions:
- Differentiate Combinational and sequential circuits.
  - Can adder be used as a Subtractor, If yes explain how?
  - Differentiate RAM and ROM.
  - What is a multiplier?
  - Differentiate half and full adder.
  - How role of MUX is different from DEMUX?
  - Differentiate PAL & PLA.
  - Define FSM.
  - What do you mean by asynchronous inputs of Flip-flop?
  - What is the difference between latch and a flip-flop?

**PART B (5x8marks)**

- Q. 2. What do you mean by FSM? Explain its limitations. CO3  
OR  
Explain the working of Moore and Mealy machines. CO3
- Q. 3. Explain in detail the design of Sequential machine using ASM chart. CO2  
OR  
Explain ASM charts by taking suitable example. CO2
- Q. 4. Implement Full adder using 8:1 MUX. CO1  
OR  
Write note on Programmable logic devices. CO1
- Q. 5. Design a counter that count in sequence 0-1-2-3-4 and back to initial state CO4  
using D flip-flops. The counter must avoid lock-out condition.  
OR  
What is Flip-flop? Design a clocked JK Flip-flop. CO4
- Q. 6. Design a 3-bit look ahead carry adder. CO1  
OR  
Design a BCD to Excess-3 code converter using PLA. CO1