

ROLL No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total number of pages: []
Total number of questions: 06

BCA || 3rd Sem

Digital Circuits & Logic Design

Subject Code: BSBC-303

Paper ID:

(for office use)

Time allowed: 3 Hrs

Important Instructions:

Max Marks: 60

- All questions are compulsory
- Assume any missing data

PART A (2×10)

Q. 1. Short-Answer Questions:

All COs

- What is number system?
- What are logic gates?
- Explain half adder?
- Discuss Boolean algebra?
- Explain encoder and decoder?
- What is race condition?
- Define counter?
- What is SOP?
- What is Boolean expression?
- Discuss applications of flip flops?

PART B (8×5)

Q. 2. Explain with example 1's and 2's compliment methods for arithmetic operations? COa

OR

Explain logic gates with suitable examples?

COa

Q. 3. Explain K-maps with suitable examples? COb

OR

Discuss SOP and POS with examples?

COb

Q. 4. What do you mean by multiplexer and de multiplexer? Explain COc

OR

What do you mean by flip flop? Explain J-K flip flop?

COc

COd

Q. 5. Discuss counters?

OR

How synchronous and asynchronous counters designed?

COd

COe

Q. 6. Explain binary adder and sub tractor?

OR

Discuss encoders and decoders?

COe